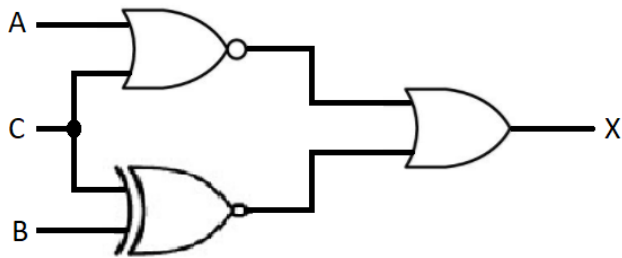


SEL0414 - Sistemas Digitais
Resolução Lista 4 - Circuitos Combinacionais

01


$$X = \overline{A}BC + A\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC = \overline{B}C(\overline{A}+A) + BC(\overline{A}+A) + \overline{A}B\overline{C} = \overline{B}C + BC + \overline{A}B\overline{C} = \overline{C}(\overline{B} + \overline{A}B) + BC = \overline{C}(\overline{B} + \overline{A}) + BC = \overline{A}C + \overline{B}C + BC = \overline{A} + C + B \oplus C$$



02

A	B	C	S
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0


$$S = \overline{A}BC + \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} = \overline{A}B(\overline{C} + C) + \overline{A}B\overline{C} + A\overline{B}\overline{C} = \overline{A}B + \overline{A}B\overline{C} + A\overline{B}\overline{C} = \overline{A}(B + B\overline{C}) + A\overline{B}\overline{C} = \overline{A}B + \overline{A}C + A\overline{B}\overline{C} = \overline{A}B + \overline{C}(\overline{A} + A\overline{B}) = \overline{A}B + \overline{A}C + \overline{B}C = \overline{A} + B + \overline{A} + C + \overline{B} + C$$

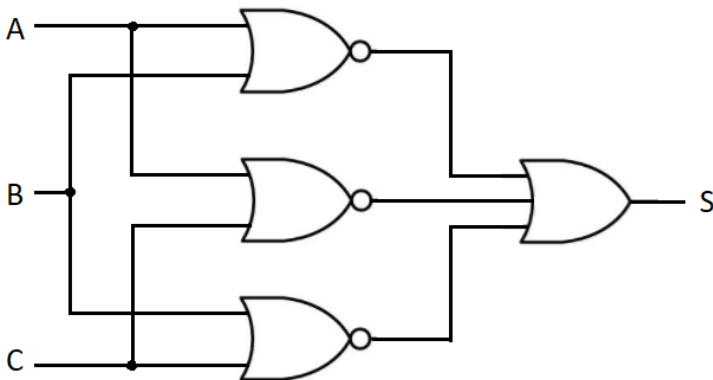

03

A_3	A_2	A_1	A_0	S
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$$\begin{aligned} \overline{A_3} \overline{A_2} A_1 A_0 + \overline{A_3} A_2 \overline{A_1} \overline{A_0} + \overline{A_3} A_2 \overline{A_1} A_0 + \overline{A_3} A_2 A_1 \overline{A_0} + \overline{A_3} A_2 A_1 A_0 &= \overline{A_3} A_1 A_0 (\overline{A_2} + A_2) + \overline{A_3} A_2 \overline{A_0} (\overline{A_1} + A_1) + \overline{A_3} A_2 A_1 A_0 \\ &= \overline{A_3} A_1 A_0 + \overline{A_3} A_2 \overline{A_0} + \overline{A_3} A_2 \overline{A_1} A_0 \overline{A_3} A_1 A_0 + \overline{A_3} A_2 (\overline{A_0} + A_1 A_0) = \overline{A_3} A_1 A_0 + \overline{A_3} A_2 \overline{A_0} + \overline{A_3} A_2 \overline{A_1} \\ &= \overline{A_3} (A_1 A_0 + A_2 \overline{A_0} + A_2 \overline{A_1}) = \overline{A_3} [A_2 (\overline{A_1} + \overline{A_0}) + A_1 A_0] = \overline{A_3} (A_2 \overline{A_1} \overline{A_0} + A_1 A_0) = \overline{A_3} (A_1 A_0 + A_2) \end{aligned}$$

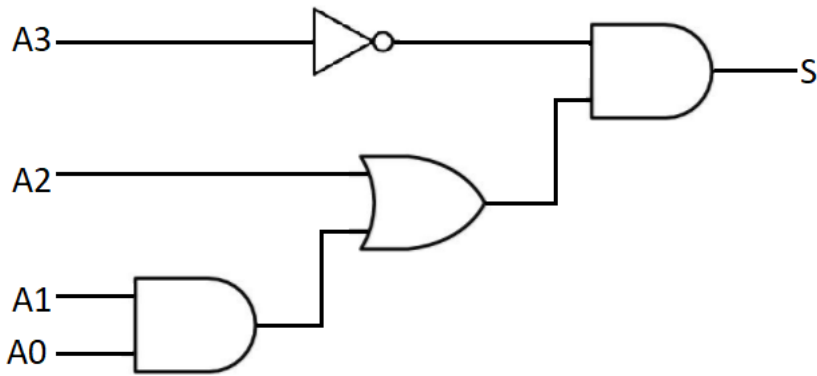

04

P	I	L	A
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$A = \overline{P}IL + P\overline{I}L + P\overline{I}\overline{L} + P\overline{I}L = \overline{I}L(\overline{P} + P) + P\overline{I}(\overline{L} + L) = \overline{I}L + P\overline{I}$$

